

# Lab 4: Invertor


Name: Jameson Stanley Date: October 15, 2025

## Objective


Design 2 inverters with different specifications utilizing NMOS and PMOS transistors. Then using spice simulations, the functionality of the inverter can be confirmed both with and without a load capacitor.

## Part I – SCHEMATIC



Inverter 1 – 12u/6u (PMOS) / 6u/6u (NMOS)

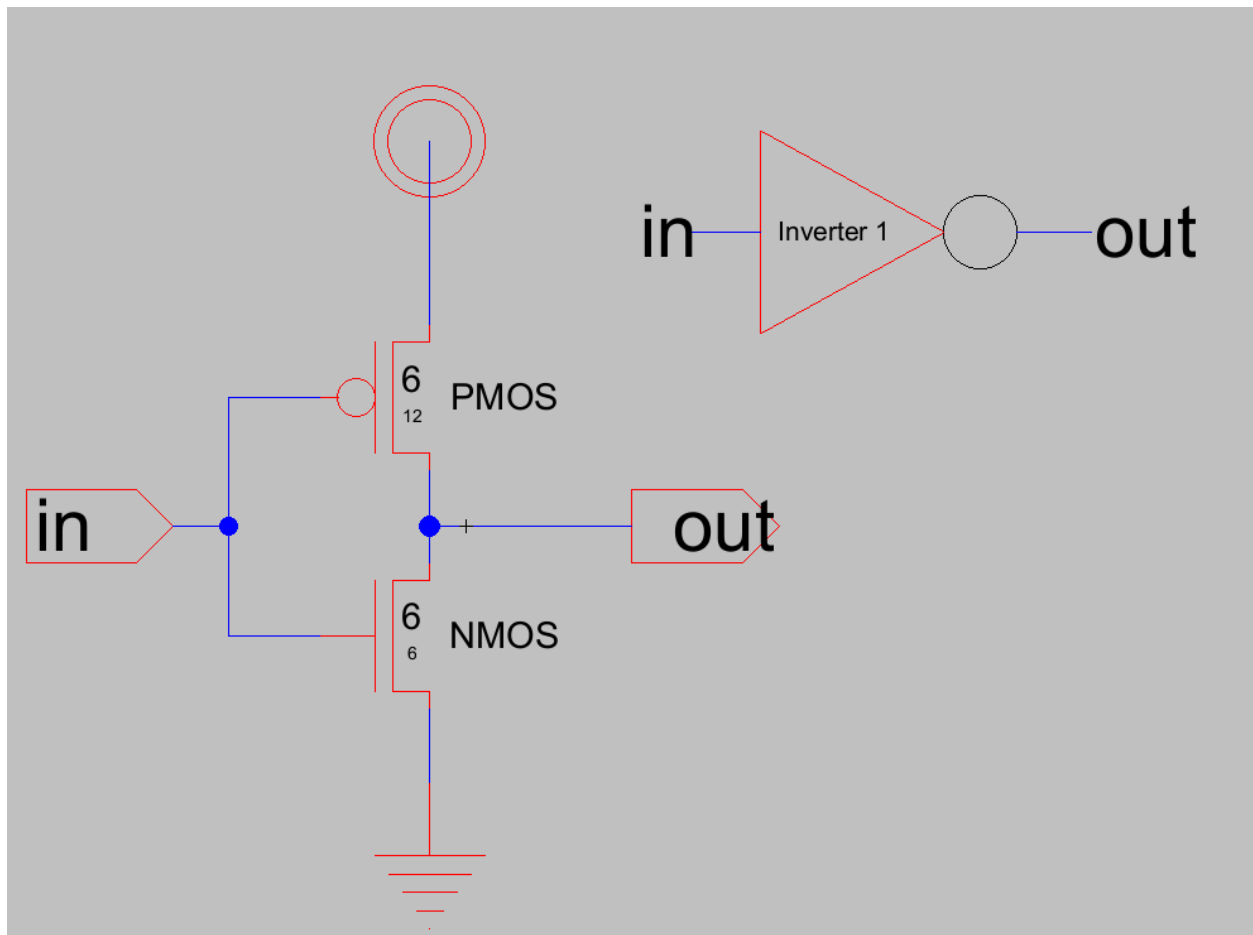

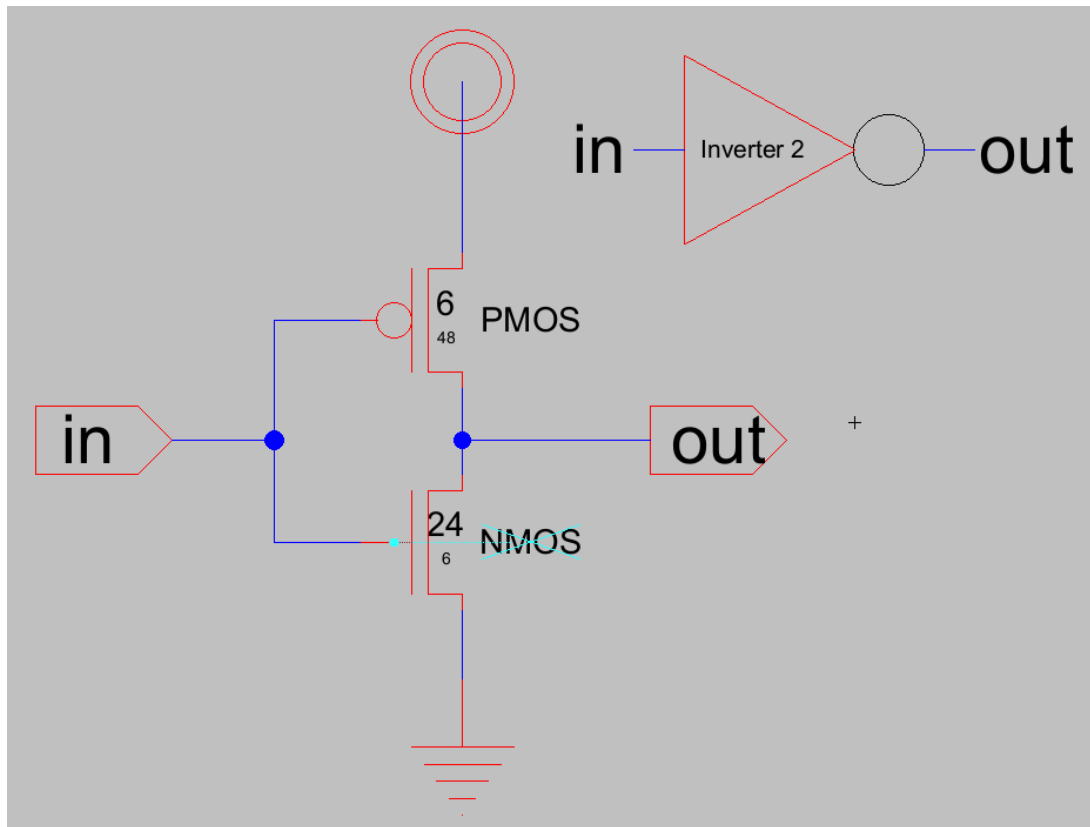
Inverter 2 – 48u/6u (PMOS) / 24u/6u (NMOS)



 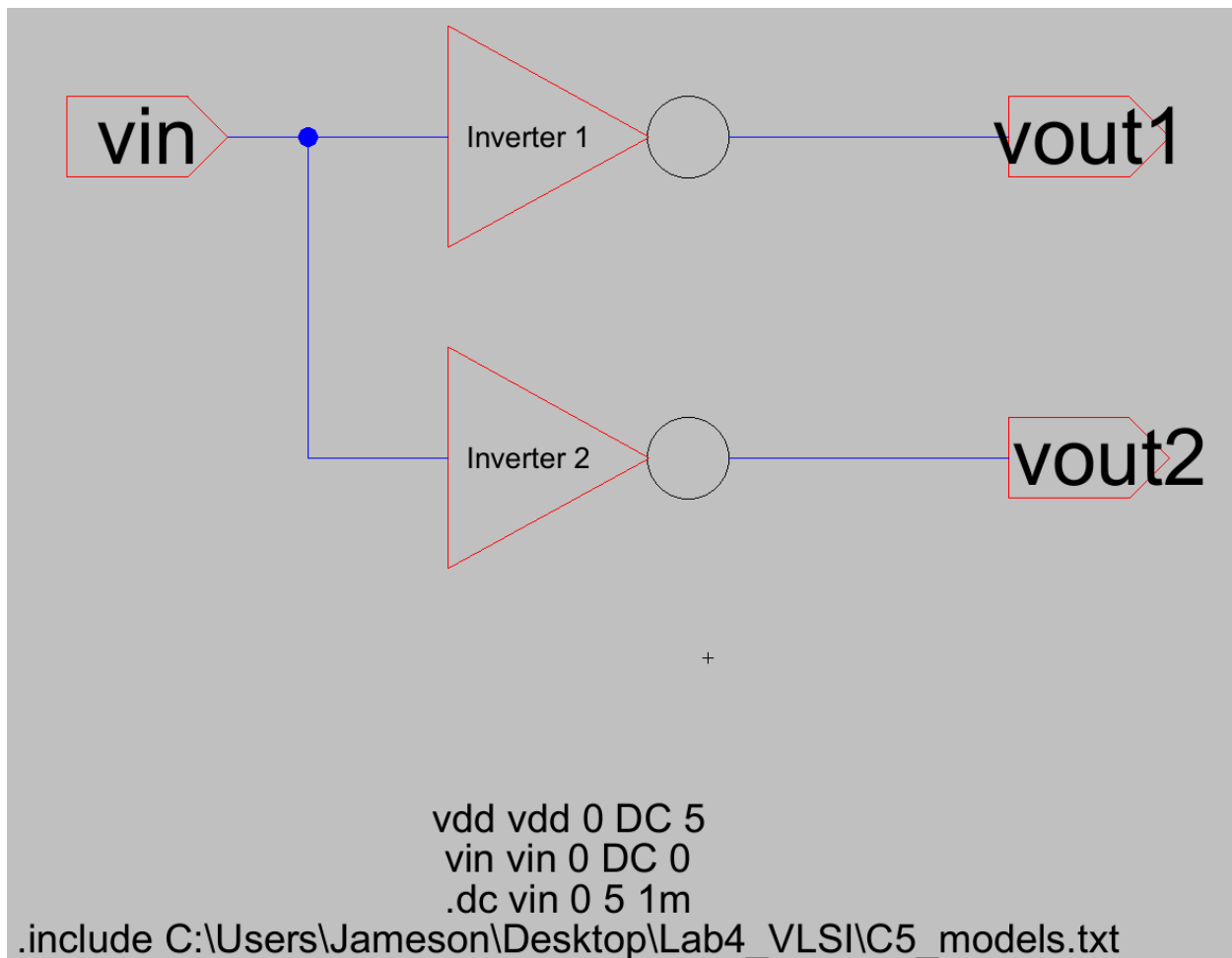
## Inverter 1 and 2 Verification schematic with Simulation




## Inverter 1 and 2 with Load Schematic

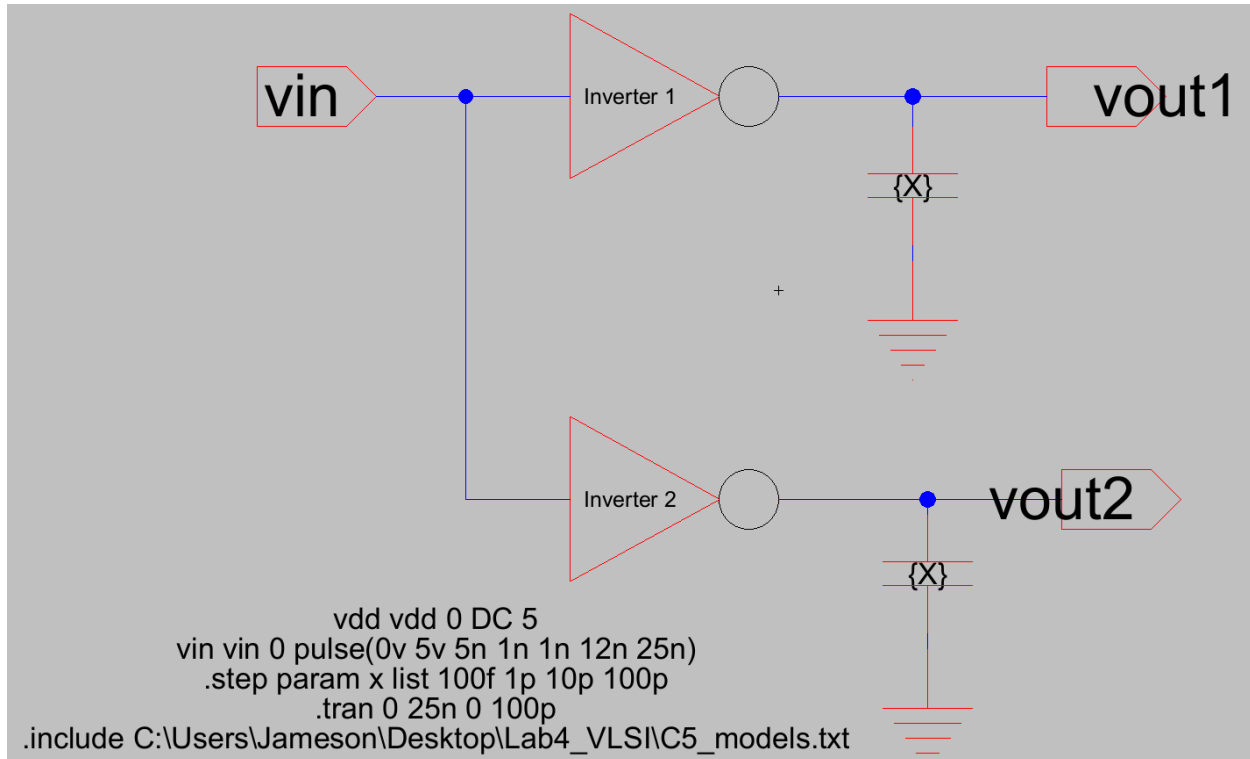

 
## Inverter 1 with load simulation (100f 1p 10p 100p)


 
## Inverter 2 with load simulation(100f 1p 10p 100p)



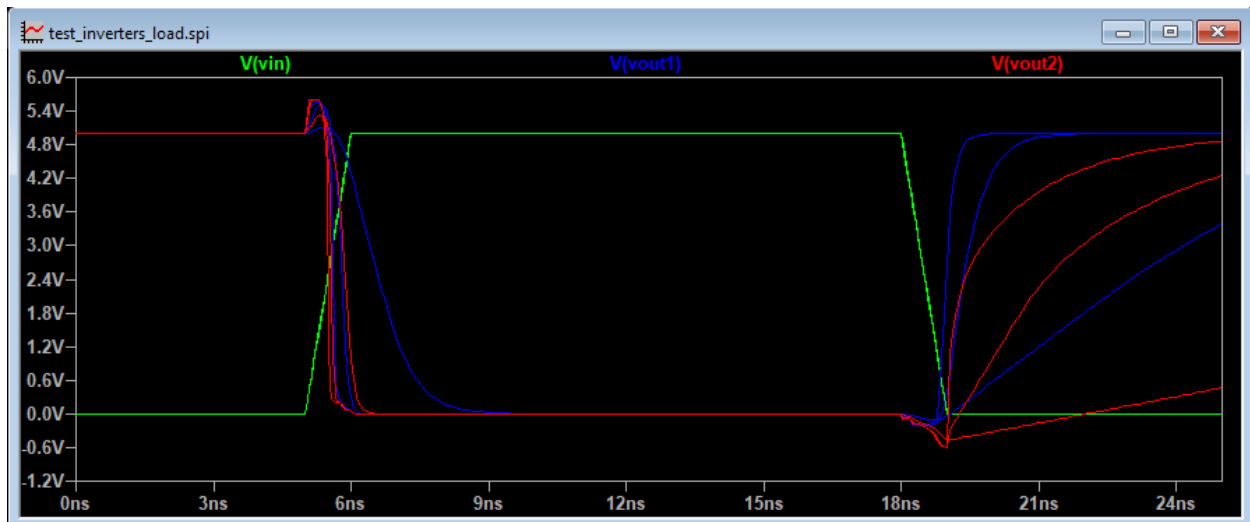
## Inverter 1 and 2 with load simulation (1f 10f 100f)



## Part II – LAYOUT

### Inverter 1 Layout with 3D View

 

### Inverter 2 Layout with 3D View

