

Lab 1 Report: 5-bit R-2R Ladder DAC

Name: Jameson Stanley

Course: VLSI Design


Date: September 25, 2025

1. Introduction

The goal is to Design a 5-R2R Ladder Dac utilizing $10\text{k}\Omega$ resistors in the Electric VLSI design software and preform simulations to confirm the functionality of the design. Then a physical layout can then be implemented using n-well resistors.

2. Schematic and Design


R_Divider Schematic

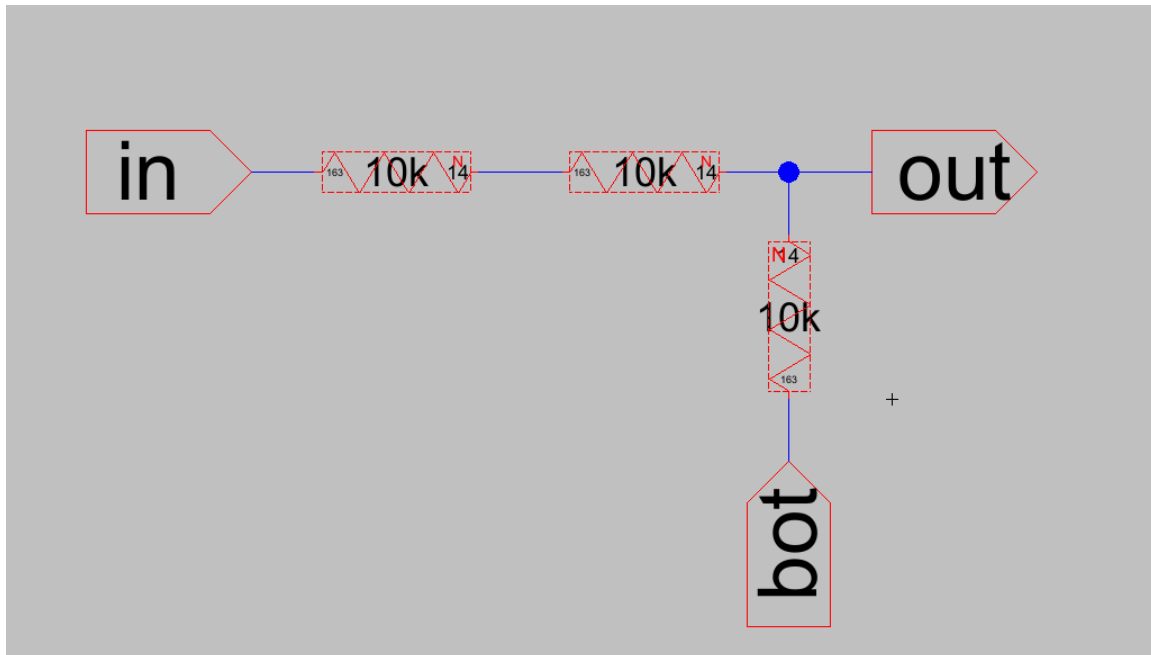

R_Divider Schematic Simulations

```
--- Operating Point ---  
  
V(vin) :      1          voltage  
V(vout) :     0.333333   voltage  
I(vin) :     -3.33333e-05 device_current  
Ix(xr_divide@1:bot) :   -3.33333e-05 subckt_current  
Ix(xr_divide@1:in) :    3.33333e-05 subckt_current  
Ix(xr_divide@1:out) :    0          subckt_current
```

5-bit DAC Schematic

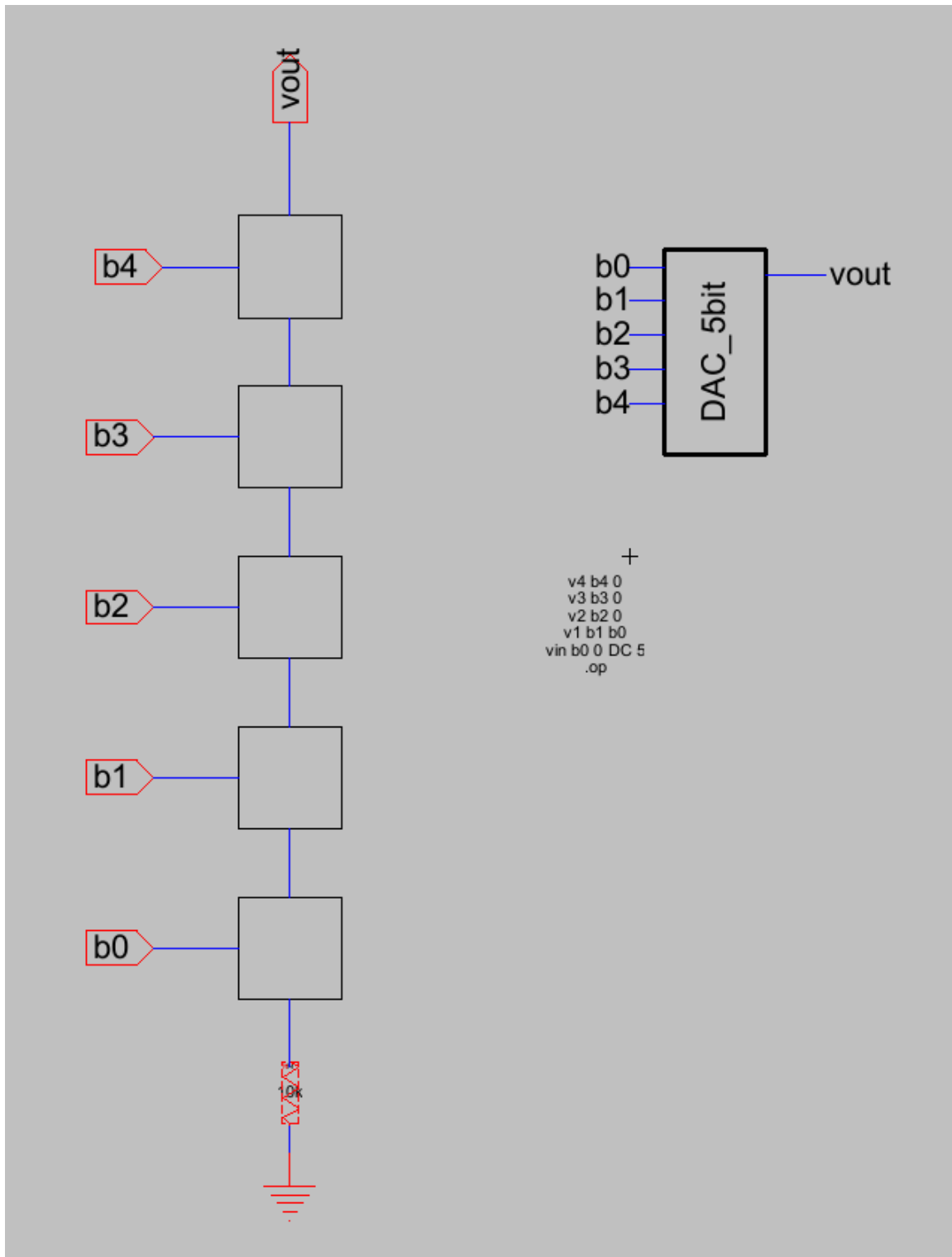


Using parallel and series reduction it can be found that the output resistance of the 5-bit DAC is roughly around $10k\Omega$.

5-bit DAC Schematic Spice simulation

```
C:\Users\Jameson\Desktop\LAB1_VLSIDESIGN\DAC_5bit.spi X
--- Operating Point ---
V(b0) :      5      voltage
V(b1) :      5      voltage
V(b2) :      0      voltage
V(b3) :      0      voltage
V(b4) :      0      voltage
V(net@0) :  2.50977  voltage
V(net@1) :  2.51953  voltage
V(net@11) :  1.25488  voltage
V(net@2) :  1.28906  voltage
V(net@3) :  0.703125  voltage
V(vout) :    0.46875  voltage
I(Rresnwell@0) : 0.000125488  device_current
I(v1) :    -0.000124023  device_current
I(v2) :    6.44531e-05  device_current
I(v3) :    3.51562e-05  device_current
I(v4) :    2.34375e-05  device_current
I(vin) :   -0.000248535  device_current
Ix(xr_divide@0:bot) : 2.34375e-05  subckt_current
Ix(xr_divide@0:in) : -2.34375e-05  subckt_current
Ix(xr_divide@0:out) : 0  subckt_current
Ix(xr_divide@1:bot) : 5.85937e-05  subckt_current
Ix(xr_divide@1:in) : -3.51562e-05  subckt_current
Ix(xr_divide@1:out) : -2.34375e-05  subckt_current
Ix(xr_divide@2:bot) : 0.000123047  subckt_current
Ix(xr_divide@2:in) : -6.44531e-05  subckt_current
Ix(xr_divide@2:out) : -5.85937e-05  subckt_current
Ix(xr_divide@3:bot) : -9.76563e-07  subckt_current
Ix(xr_divide@3:in) : 0.000124023  subckt_current
```

Delay Analysis

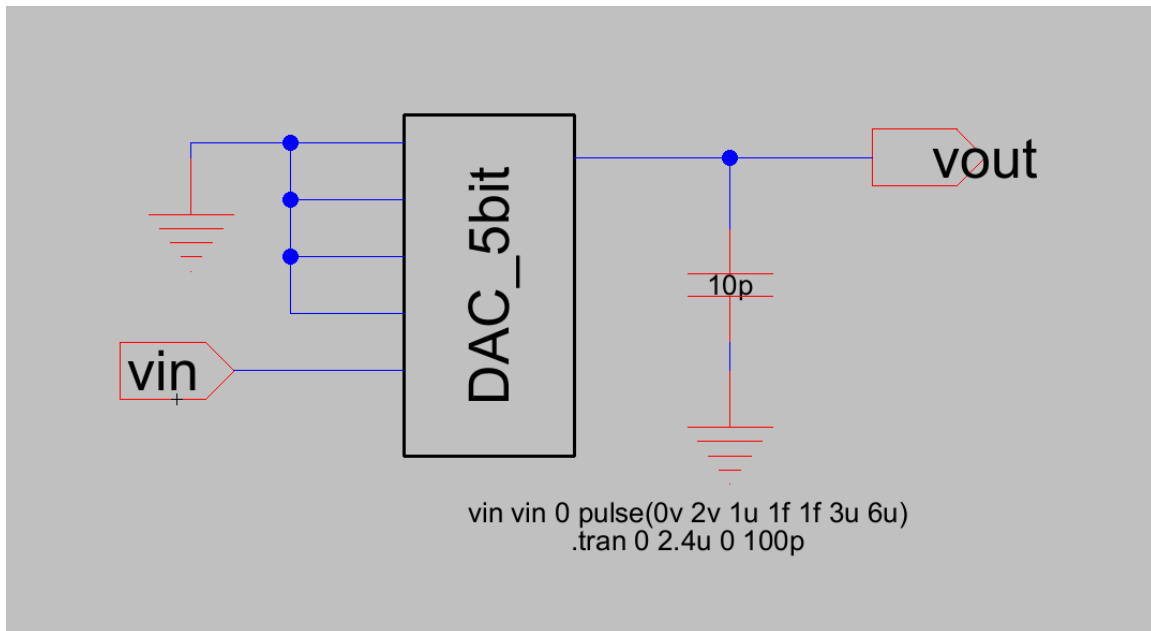


Theoretical Prediction

$$\tau = R_{\text{out}}C_L$$

$$\tau = (10\text{k}\Omega)(10\text{pF}) = 100\text{ns}$$


$$\tau_{0.7} = (100\text{ns})(0.7) = 70\text{ns}$$

Actual Analysis

 

3. Layout

R_Divider Layout

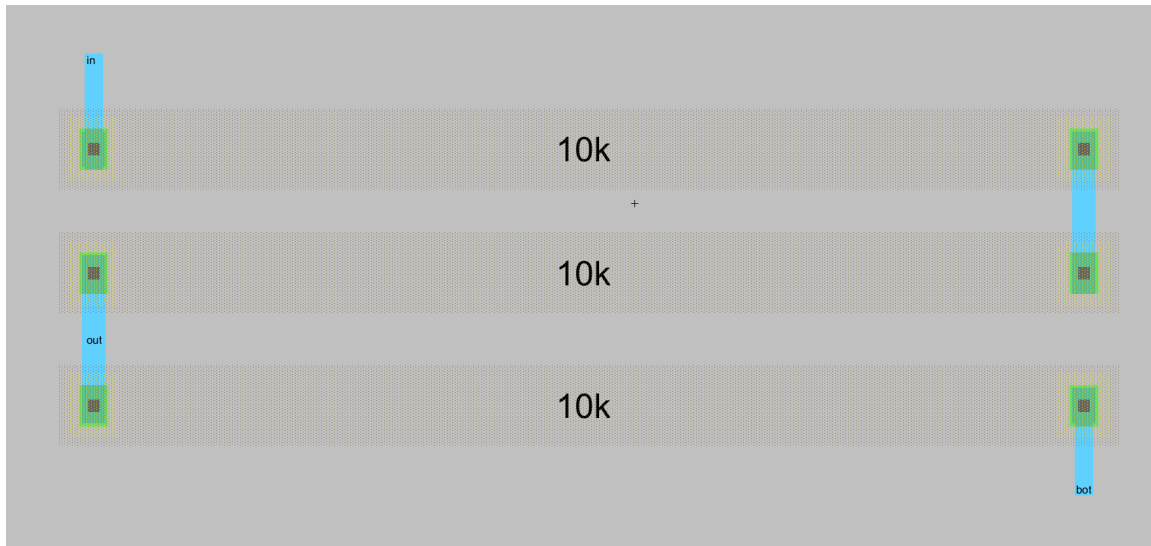

R_Divider Layout Simulation

```
--- Operating Point ---  
  
V(vin) :      1          voltage  
V(vout) :    0.333333    voltage  
I(vin) :    -3.33333e-05 device_current  
Ix(xr_divide@1:bot) : -3.33333e-05 subckt_current  
Ix(xr_divide@1:in) :  3.33333e-05 subckt_current  
Ix(xr_divide@1:out) :  0          subckt_current
```

N-Well Resistor Design


To find the dimensions required for a $10k\Omega$ the equations $R = R_{sq} * \frac{L}{W}$ can be used knowing that $R_{sq} = 855 \frac{\Omega}{sq}$ and using a chosen width of $14 \mu m$ to find the length required for a $10k\Omega$ n-well resistor.

$$R = R_{sq} * \frac{L}{W}$$
$$10k\Omega = 855 \frac{\Omega}{sq} * \frac{L}{14\mu m}$$


$$\frac{10k\Omega}{855 \frac{\Omega}{sq}} * 14\mu m = L$$

$$L \approx 16$$

3.2 DAC Layout

 

DAC Driving a 10kΩ Load

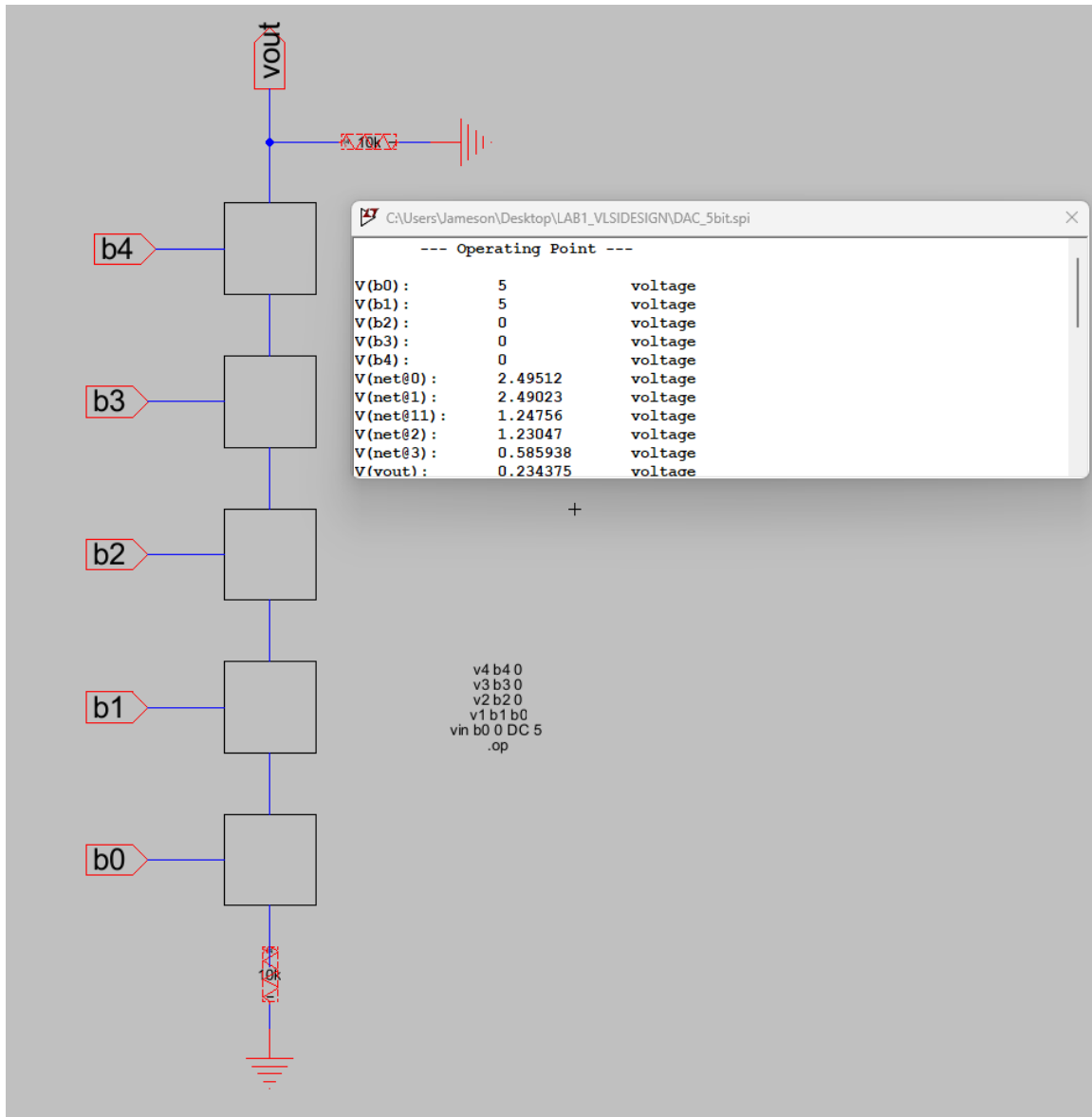

When driving a 10kΩ load the output voltage is half the original amount. This is caused due to the output resistance of the DAC being 10kΩ causing the 10kΩ load to act like a voltage divider, using the formula of a voltage divider that can be confirmed.

$$V_{out} = V_{in} \left(\frac{R_2}{R_1 + R_2} \right)$$

entering in the values $R_2 = 10k\Omega$ $R_1 = 10k\Omega$ V_{in}

DRC & LVS Results

Passed DRC & LVS

References

Electric VLSI